

# Labb 1

Alexander Benteby



## Arduino code for task 1&2

```
int gate3 = 3;
int gate4 = 4;
int led = 1;
void setup() {
  // put your setup code here, to run once:
  pinMode(led, OUTPUT);
  pinMode(gate3, OUTPUT);
  pinMode(gate4, OUTPUT);
}
void loop() {
  // put your main code here, to run repeatedly:
  digitalWrite(gate3, LOW);
  digitalWrite(gate4, LOW);
  redBlink();

  digitalWrite(gate3, HIGH);
  digitalWrite(gate4, LOW);
  redBlink();
  digitalWrite(gate3, LOW);
  digitalWrite(gate4, HIGH);
  redBlink();
  digitalWrite(gate3, HIGH);
  digitalWrite(gate4, HIGH);
  delay(7000);
  return;
}
void redBlink(){
  delay(2000);
  digitalWrite(led, HIGH);
  delay(200);
  digitalWrite(led, LOW);
  delay(200);
  digitalWrite(led, HIGH);
  delay(200);
  digitalWrite(led, LOW);
}
```

what the code does is simply try all combinations for the inputs and between every combination, the red lamps blink twice so you easily can see how the circuit preforms.

### code for second part on task 3:

```
int gate3 = 3;
int gate4 = 4;
int gate0 = 0;
int gate2 = 2;
int led = 1;
void setup() {
  // put your setup code here, to run once:
  pinMode(gate3, OUTPUT);
  pinMode(gate4, OUTPUT);
  pinMode(gate2, OUTPUT);
  pinMode(gate0, OUTPUT);

  pinMode(led, OUTPUT);
}
void loop() {
  // put your main code here, to run repeatedly:
  redBlink();

  digitalWrite(gate3, LOW);
  digitalWrite(gate4, LOW);
  digitalWrite(gate2, LOW); //output: yellow 0, red 0, yellow 0
  digitalWrite(gate0, LOW);
  redBlink();

  digitalWrite(gate3, HIGH); //output: yellow 0, red 1, yellow 0
  digitalWrite(gate4, LOW);
  digitalWrite(gate2, LOW);
  digitalWrite(gate0, LOW);
  redBlink();

  digitalWrite(gate3, LOW); //output: yellow 0, red 1, yellow 0
  digitalWrite(gate4, LOW);
  digitalWrite(gate2, HIGH);
  digitalWrite(gate0, LOW);
  redBlink();

  digitalWrite(gate3, HIGH); //output: yellow 1, red 0, yellow 0
  digitalWrite(gate4, HIGH);
  digitalWrite(gate2, LOW);
  digitalWrite(gate0, LOW);
  redBlink();
```

```

digitalWrite(gate3, HIGH); //output: yellow 1, red 1, yellow 0
digitalWrite(gate4, HIGH);
digitalWrite(gate2, HIGH);
digitalWrite(gate0, LOW);
redBlink();



digitalWrite(gate3, HIGH); //output: yellow 1, red 0, yellow 1
digitalWrite(gate4, HIGH);
digitalWrite(gate2, HIGH);
digitalWrite(gate0, HIGH);

delay(7000);
return;
}
void redBlink(){
  delay(2000);
  digitalWrite(led, HIGH);
  delay(200);
  digitalWrite(led, LOW);
  delay(200);
  digitalWrite(led, HIGH);
  delay(200);
  digitalWrite(led, LOW);
}


```

this code is similar to the previous only we added another 2 outputs from the trinket, gate0 and gate2.

## Task 1:

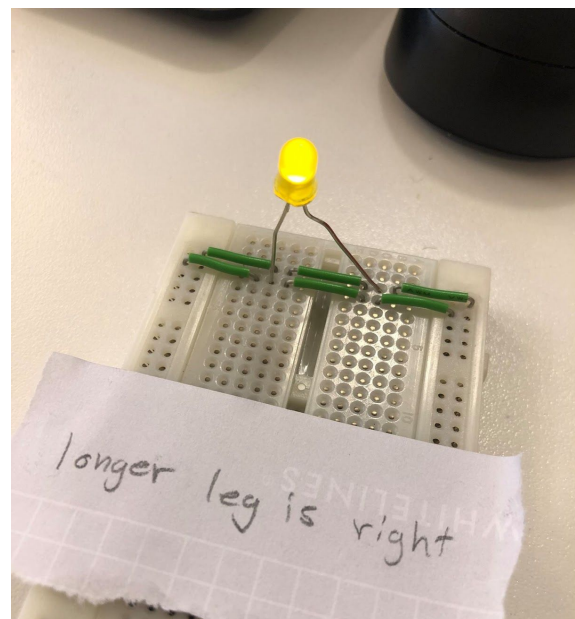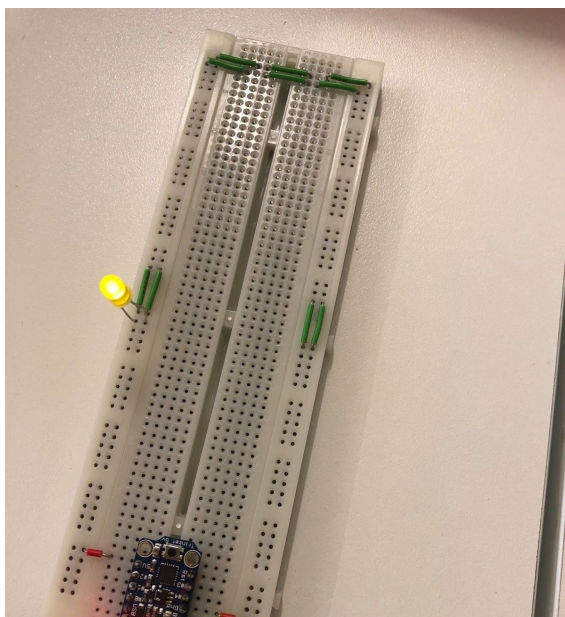


setting up as figure 1 a)

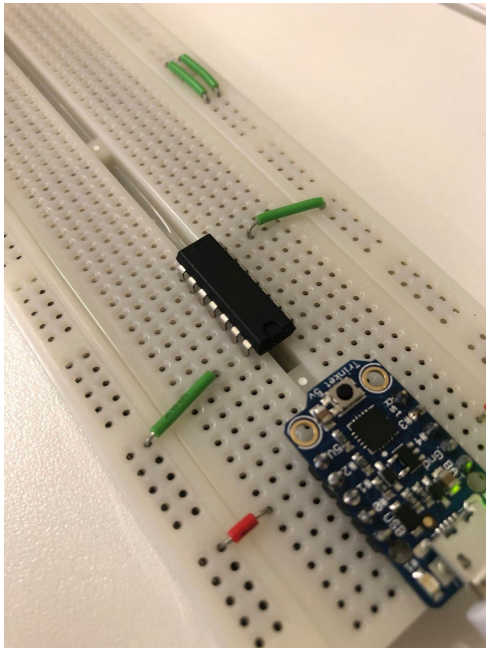

7400 series chip in middle being powered.


the vertical wires provide +- flow

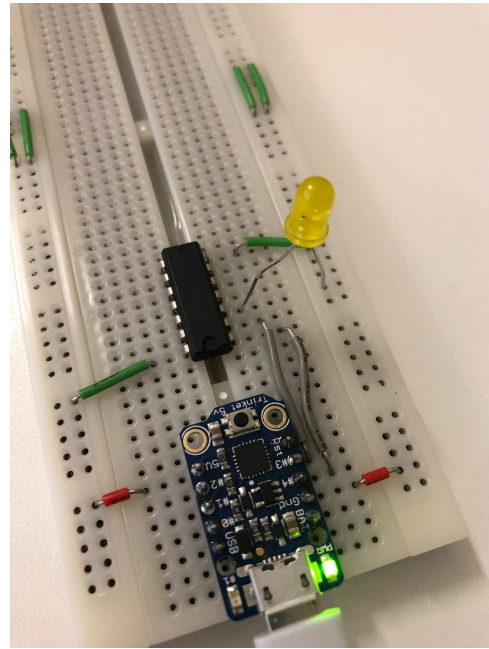


similar setup to figure 1 b)

We run the code provided in the beginning of the code and we get appropriate response from the led.  $3 \& 4 = 0$ : led=0, 3 or 4=1: led =1.

## Task 2:

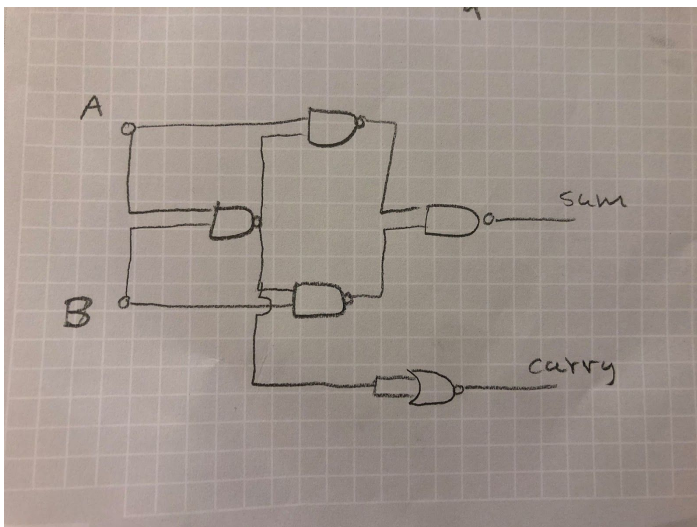

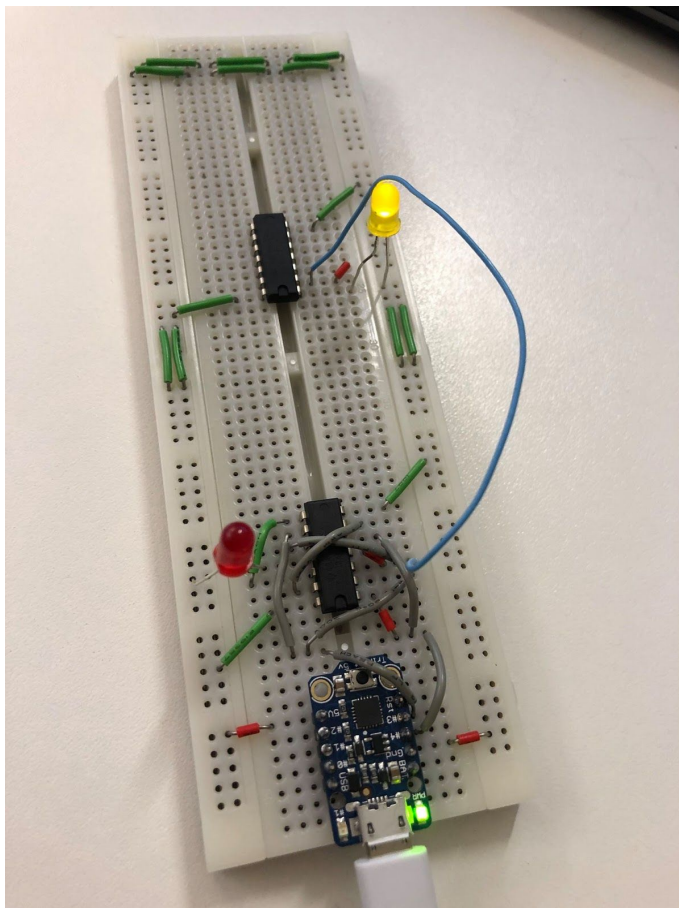The design i choose to create a halfadder with 4 NAND and 1 NOR



Added a 7402 series chip to create the halfadder. red led is the sum and yellow led is the carry. it works properly.


resulting output:

input 3	input 4	sum output	carry output
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1


## Task 3:

my Or gate:




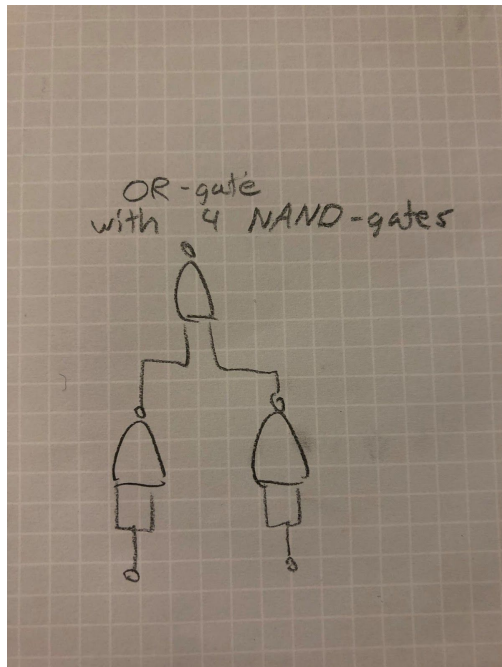


my design of an or-gate

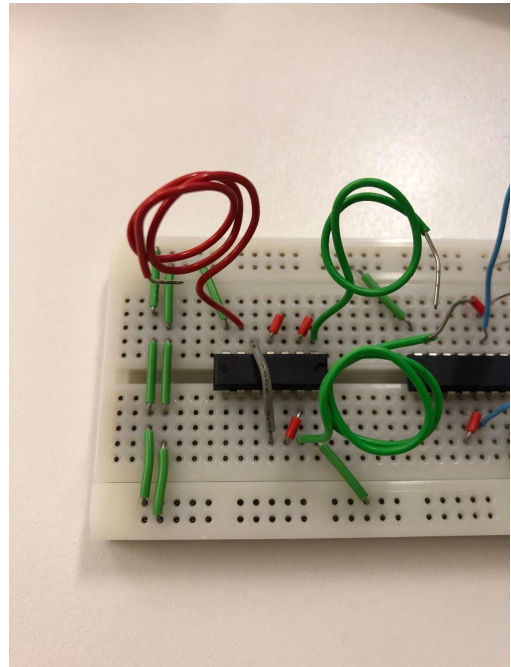

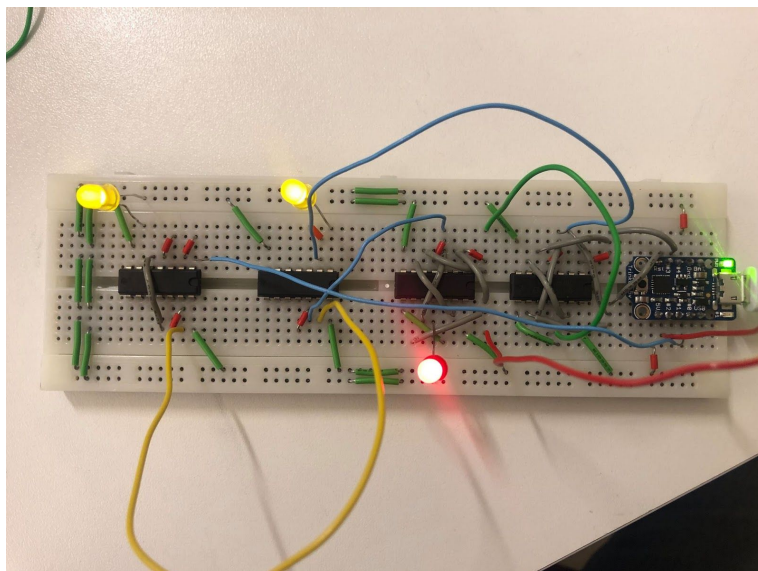green wires show input, red wire shows output.



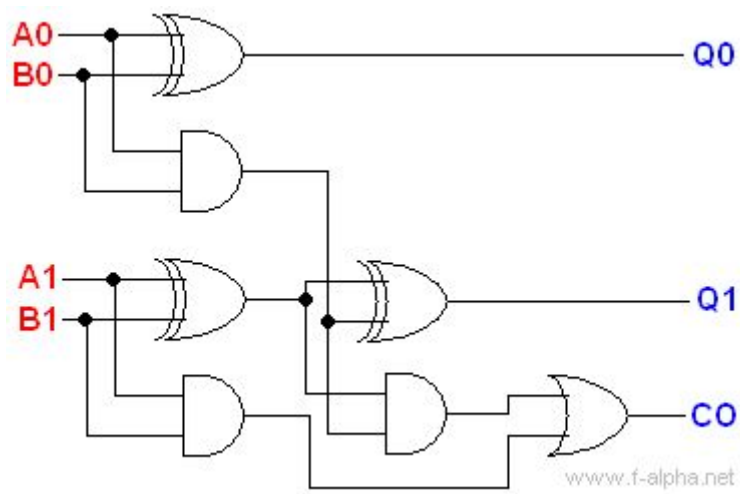I followed the example below to construct the part above.



I use gate 0,2,3 and 4. the output was almost correct, except when adding  $11 + 11$ , then all the leds was lit up